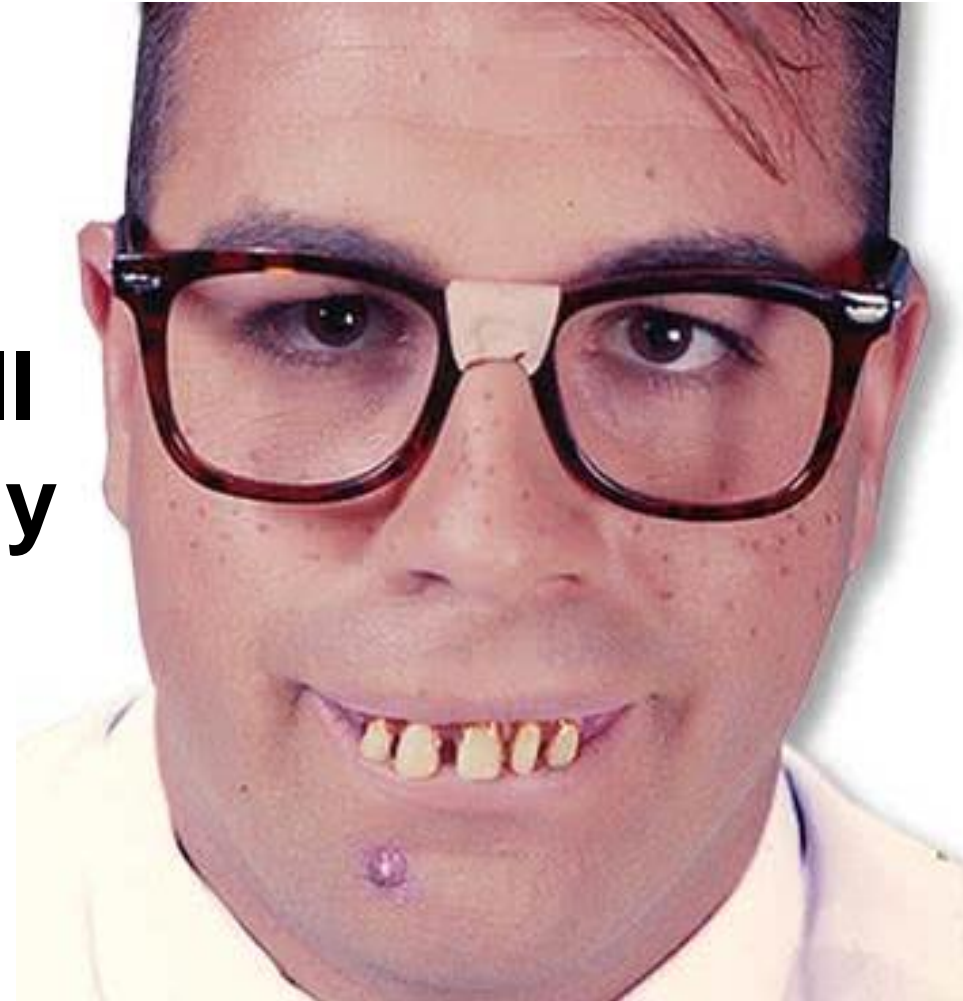


Simple Route Switching for Yards

**This presentation will
be just a little bit nerdy**

**- but fear not, no
supercalafragalisticexpialadocious
big words**



Simple Route Switching for Yards

Jim Ironside

Mini-Meet Clinic

Calgary Model Railway Society

14 Oct 2018

Why Bother?????







Aim

**To present a (relatively)
simple and inexpensive
way to operate track
routes, rather than setting
turnouts one at a time**

What is the problem?

- Yard throats/ ladders contain many turnouts**
- Usually requires setting more than one turnout to get to destination track**

Routes in a Three Track Yard

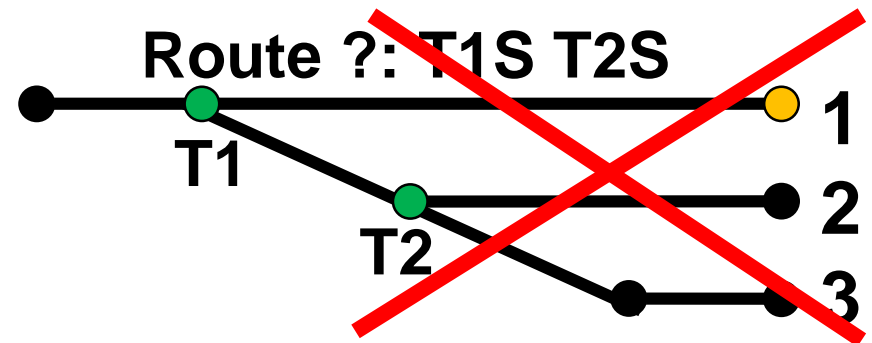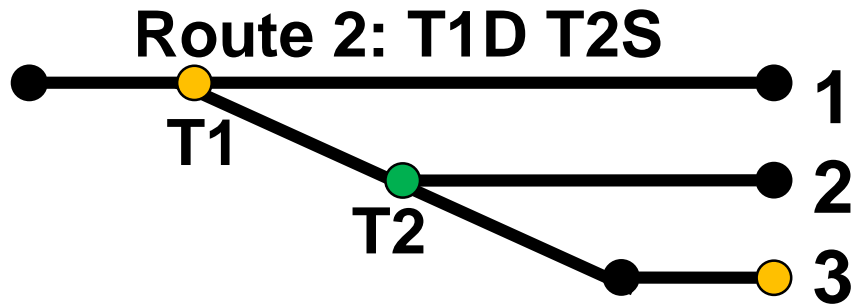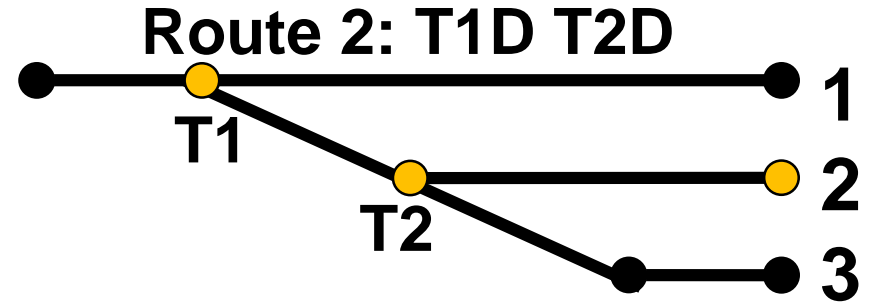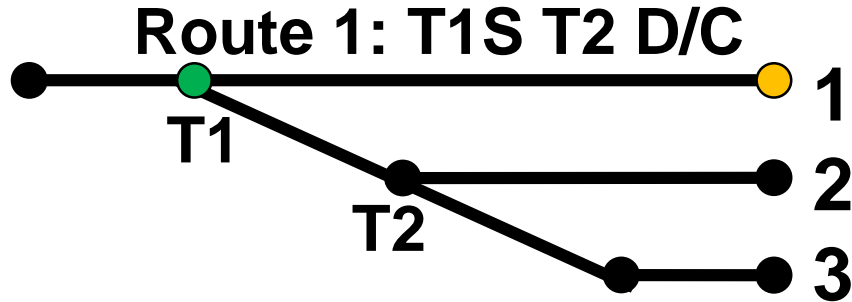


**This one is not an actual
different route**


How does a Tortoise work

Connect one way, it goes one way

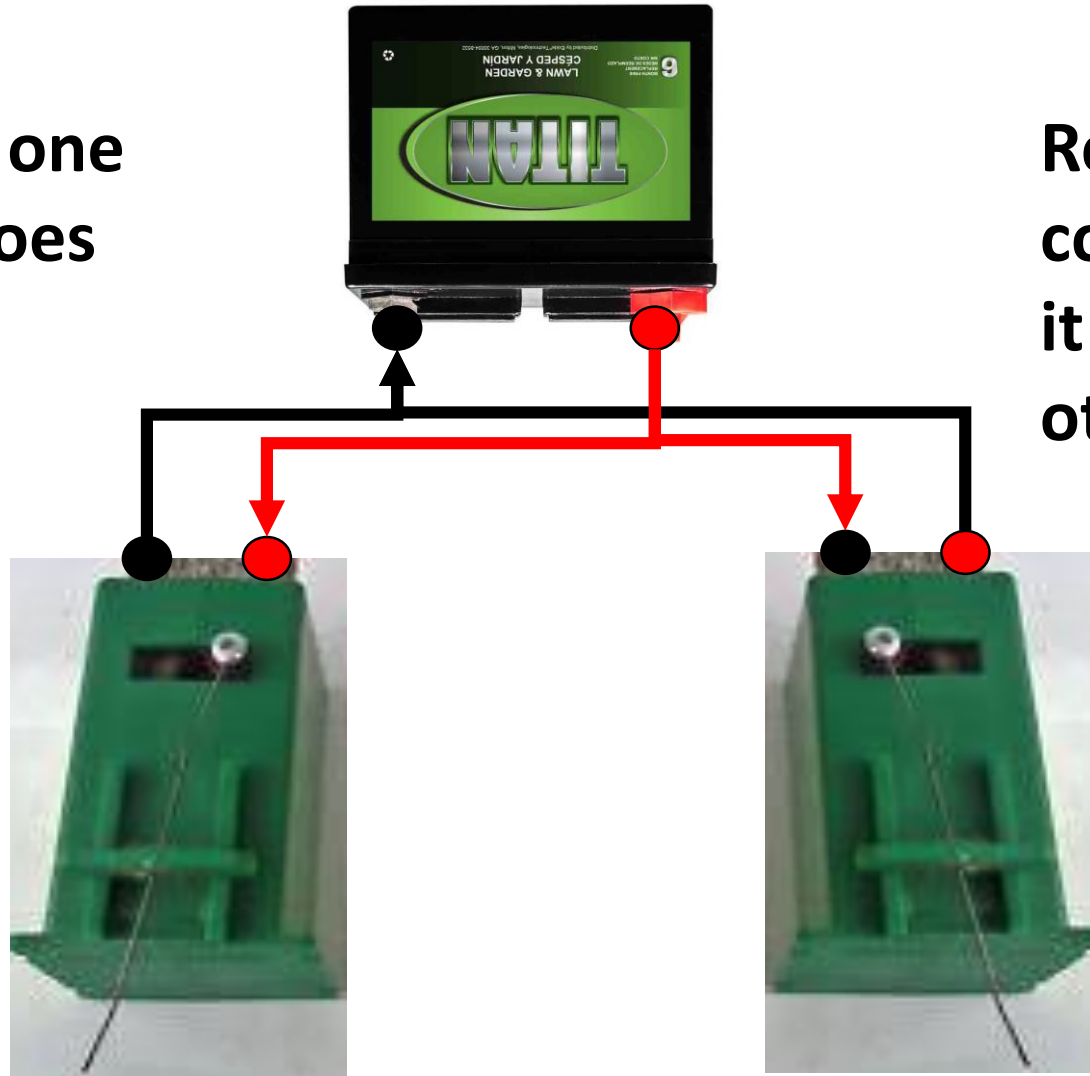Reverse connections, it goes the other way




Put a switch in between . . .

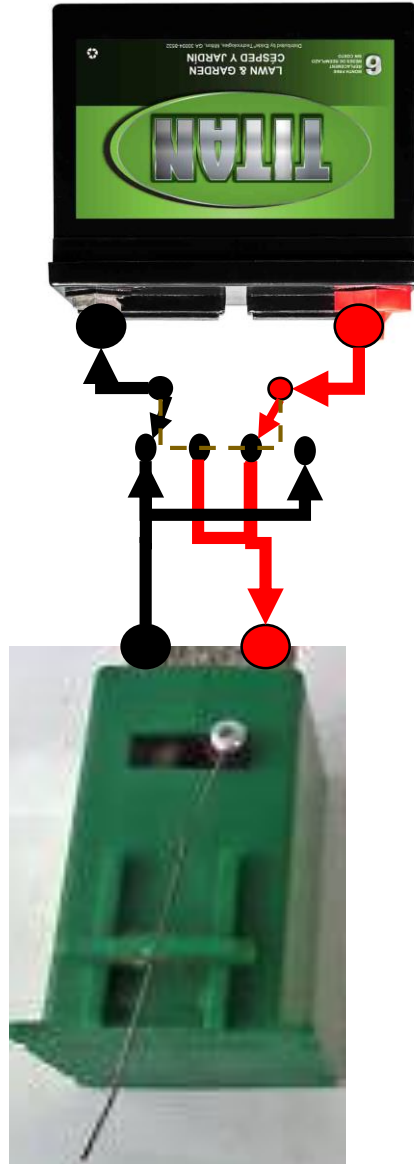


Put a DPDT
toggle in, we
can throw it
both ways

Put two switches to two Tortoises. . .


Both must
be set to
set a route

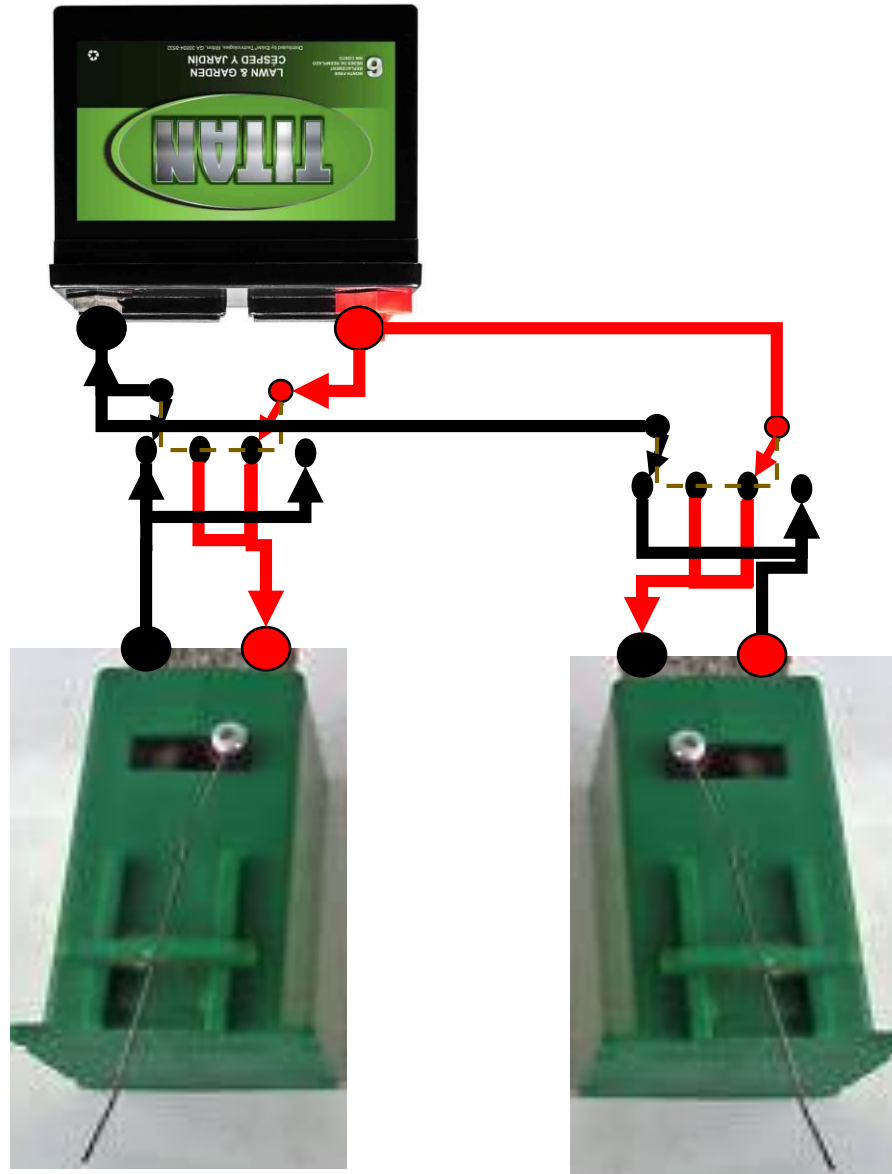

We would like something easier . . .

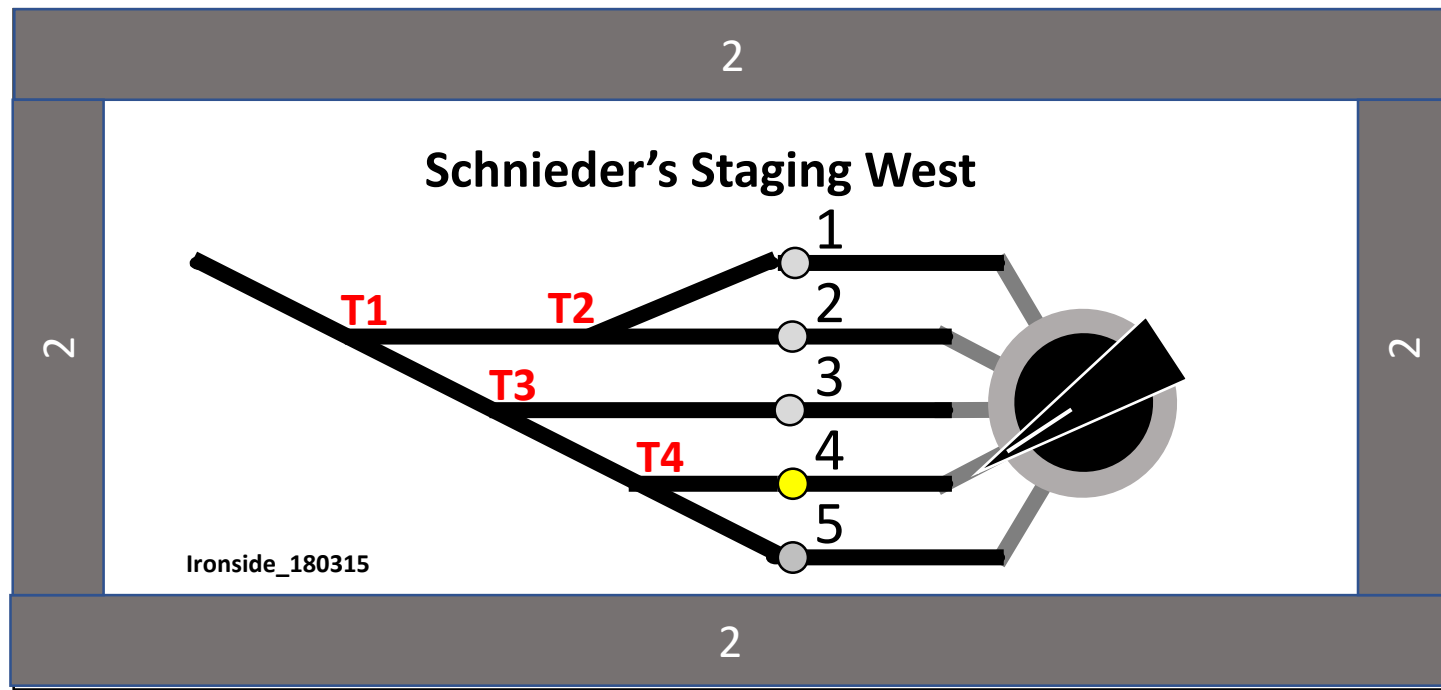

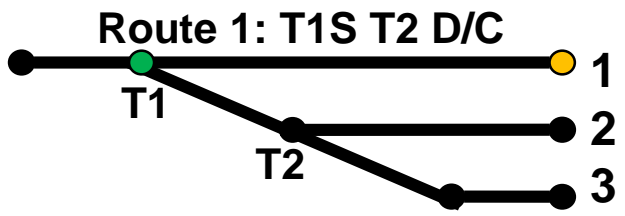- Dial desired track
 - Turnouts automatically align
- Usually requires expensive, complex controller and programming




Looking at our
three track yard

...




Dial Route 1

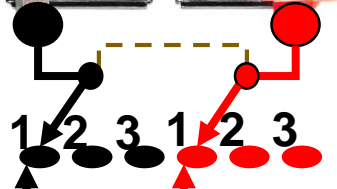


Route 1:
T1 Straight
T2 Don't Care




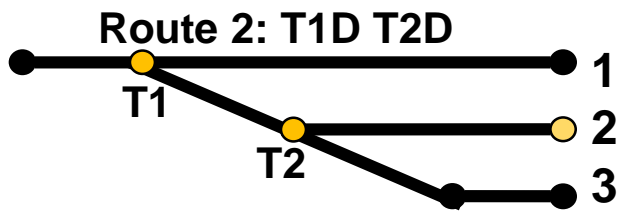

Route 2:
T1 Diverging
T2 Diverging


Dial Route 2

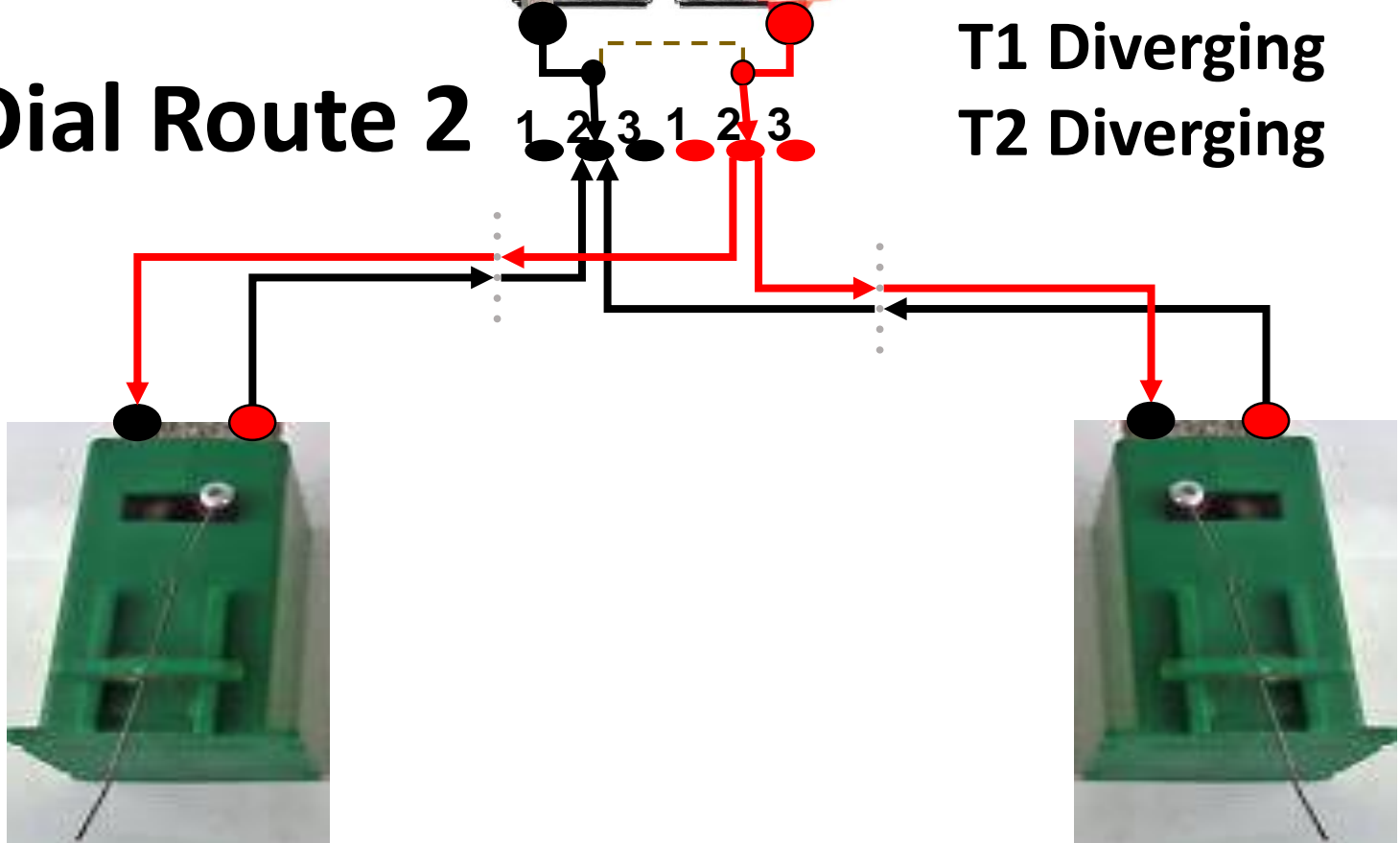

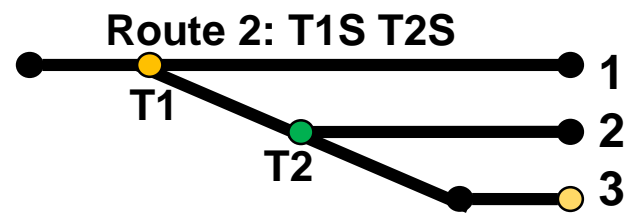


Route 3:
T1 Diverging
T2 Straight


Dial Route 3

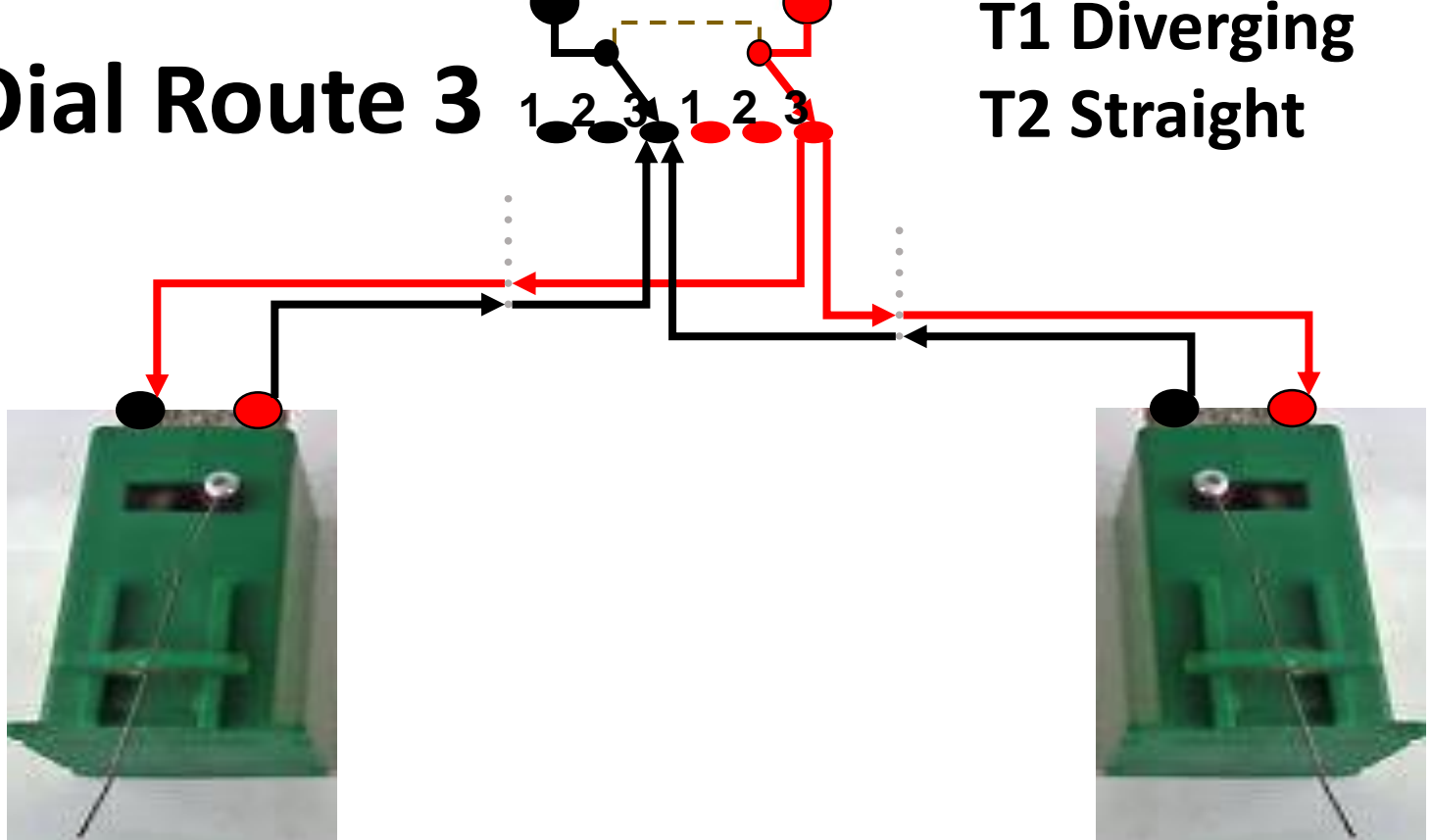


Route 1: T1S T2 D/C

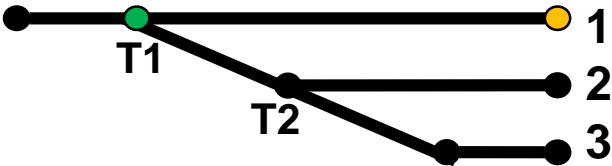

Route 2: T1D T2D

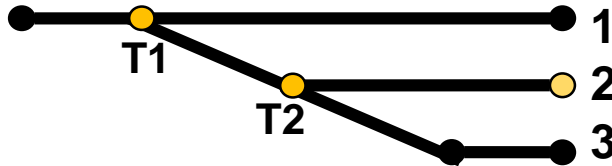





Route 2: T1S T2S

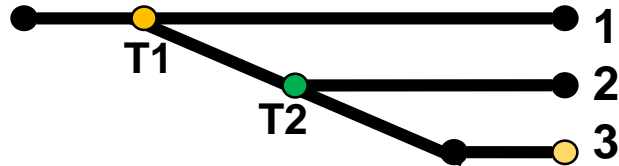

Adding up
all those
wires

Piece of
cake !!!

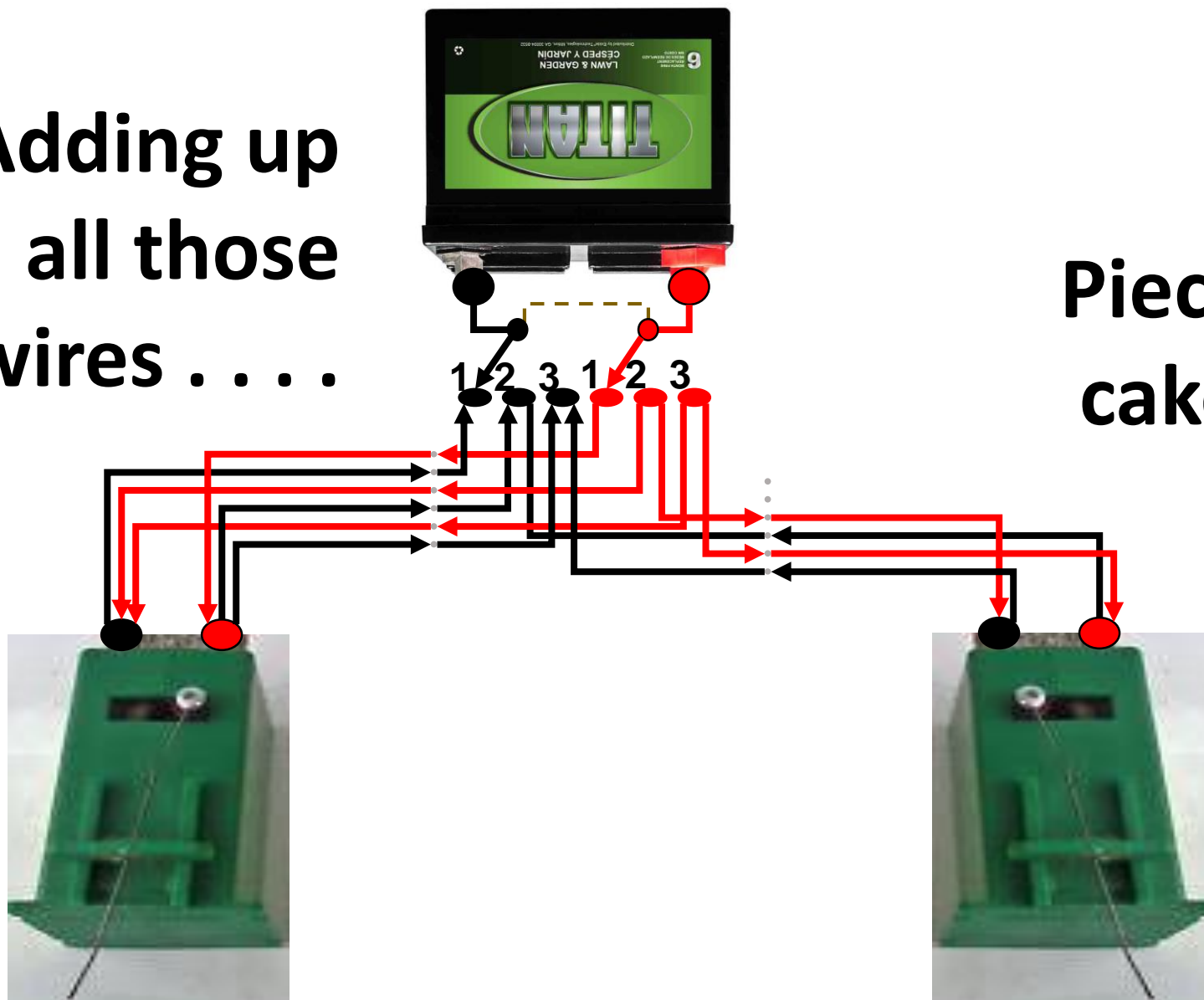

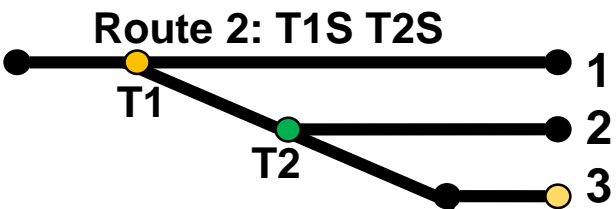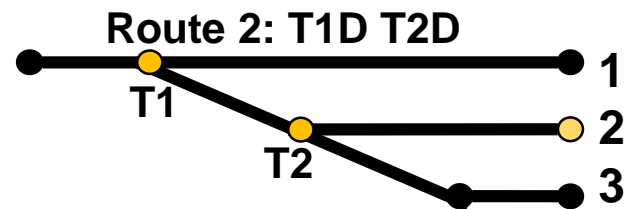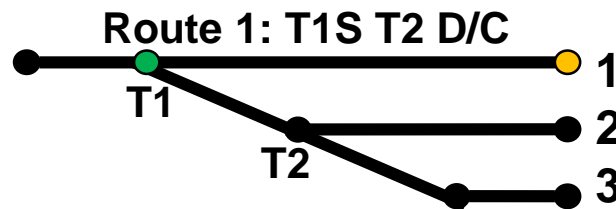


Oh Oh!!!!

Heavy purple lines allow current flow in wrong direction



Sneak Paths

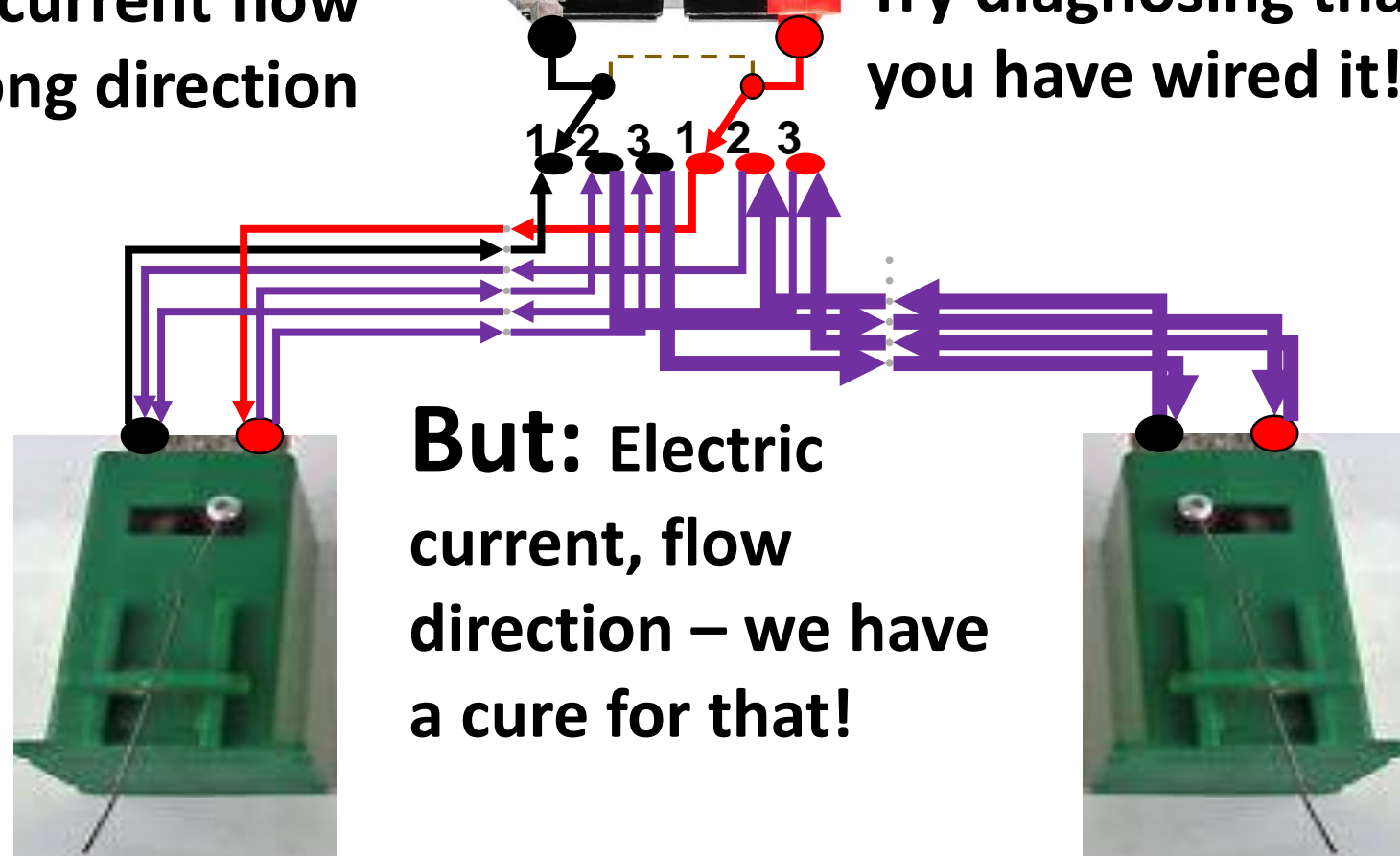create short circuits
Try diagnosing that after you have wired it!!!



But: Electric current, flow direction – we have a cure for that!



Simple Route Approach

- Complex controller – **NOT SO**
- Turnouts powered by machines go one **direction** or other depending on polarity of voltage applied, eg **direction** of electrical current
- Simple diodes control the **direction** of an electrical current


Direction - Direction - there is a solution here!!!

How does a diode work?


Diodes pass electric current in one direction, block it in the other

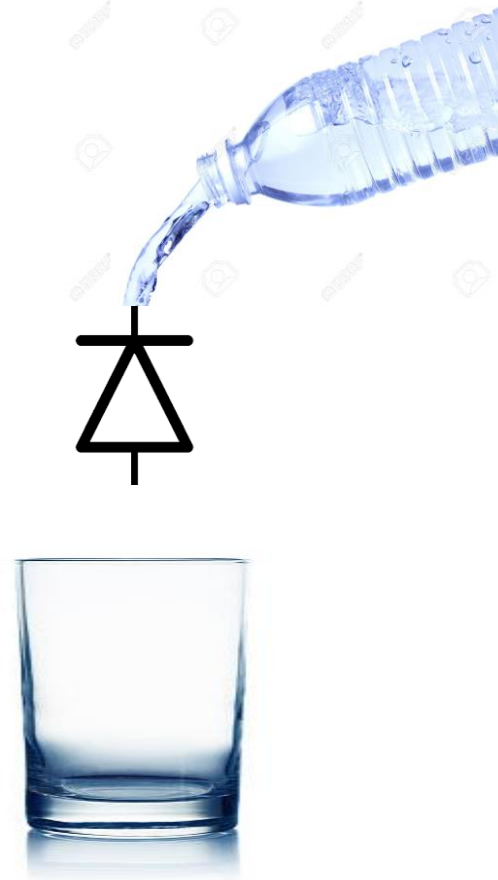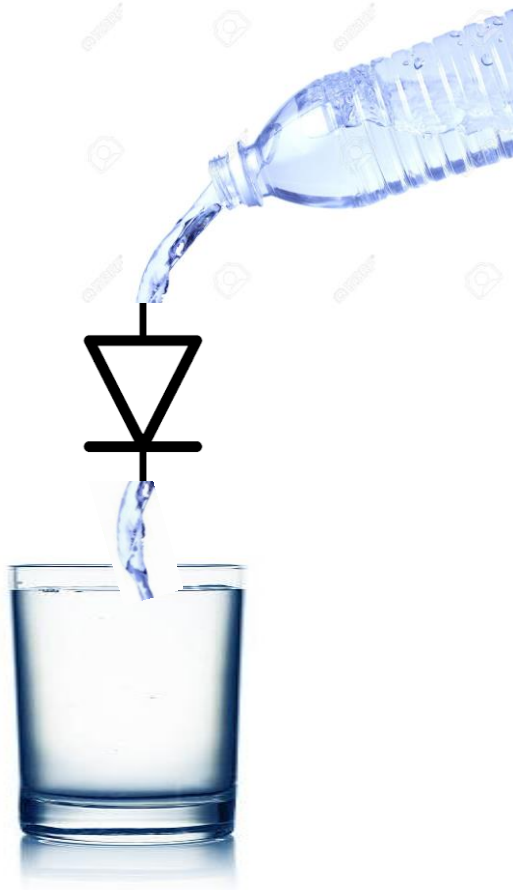


Route 1: T1S T2 D/C

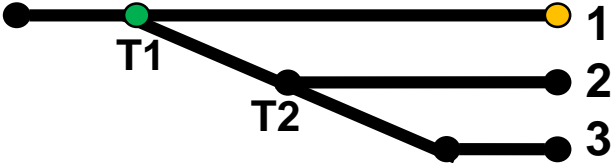

Route 2: T1D T2D

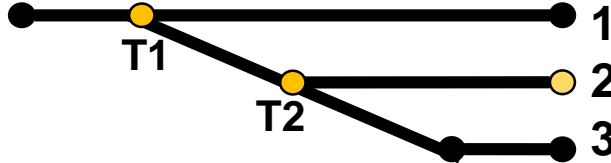





Route 2: T1S T2S

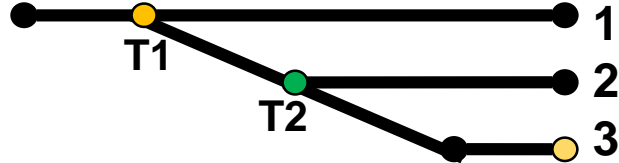

Diodes ensure current flows only in direction we want it to flow

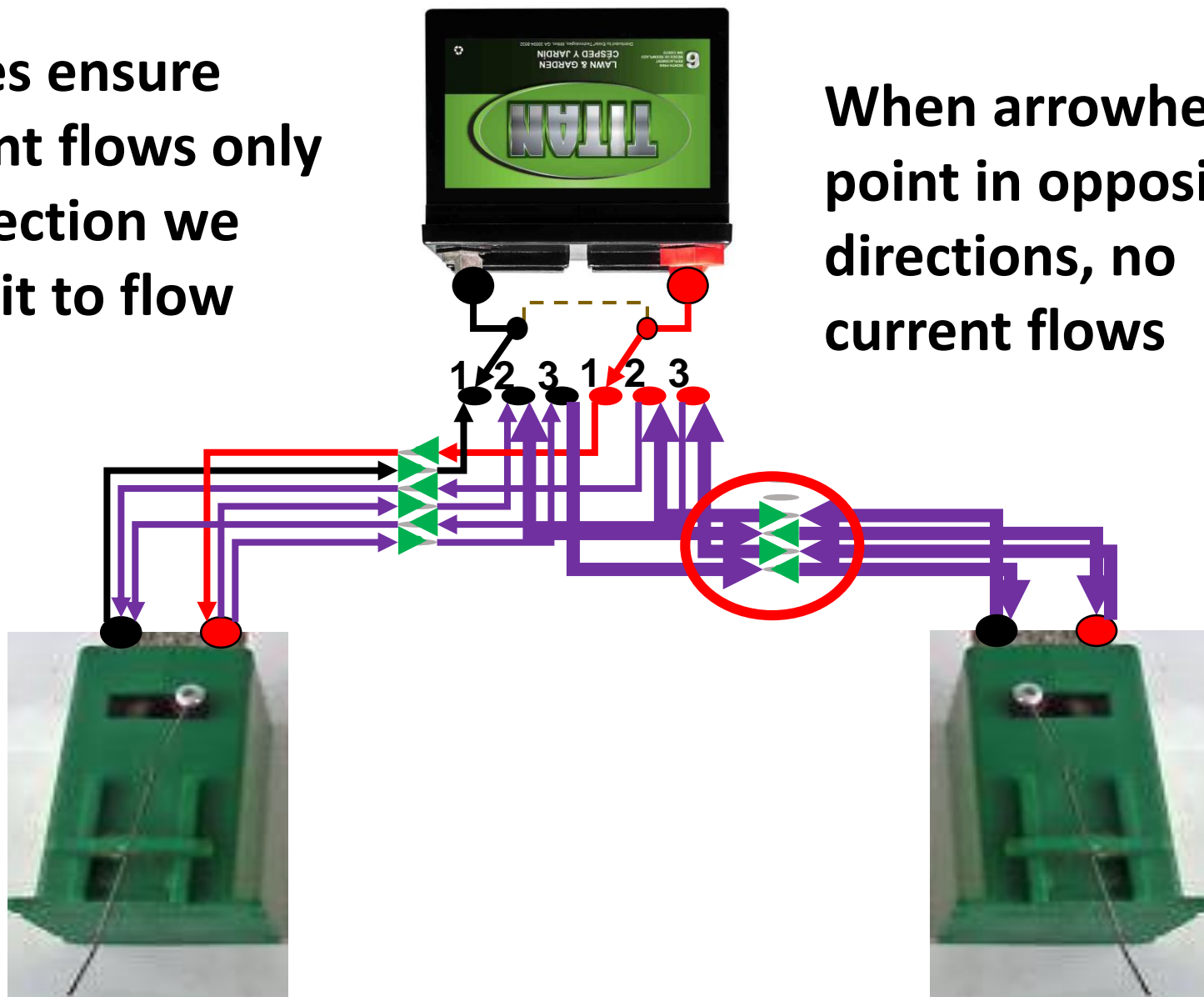
When arrowheads point in opposite directions, no current flows



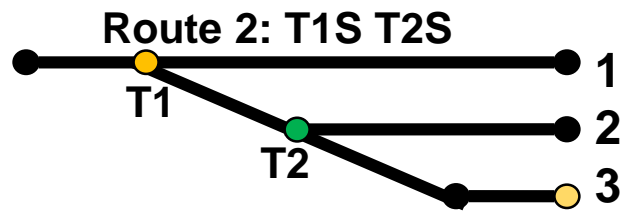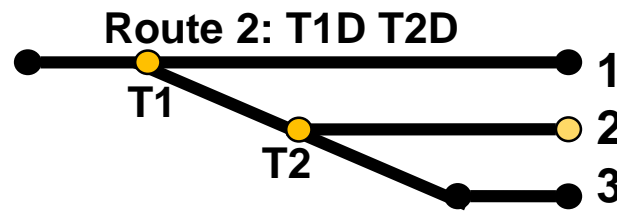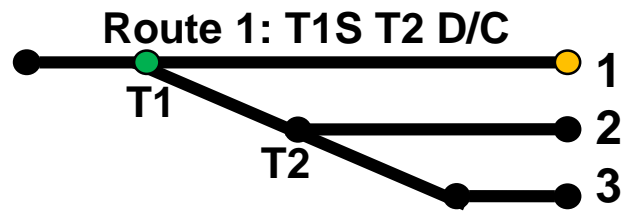

**Diodes prevent backwards flowing current
Thus those paths effectively no longer exist**

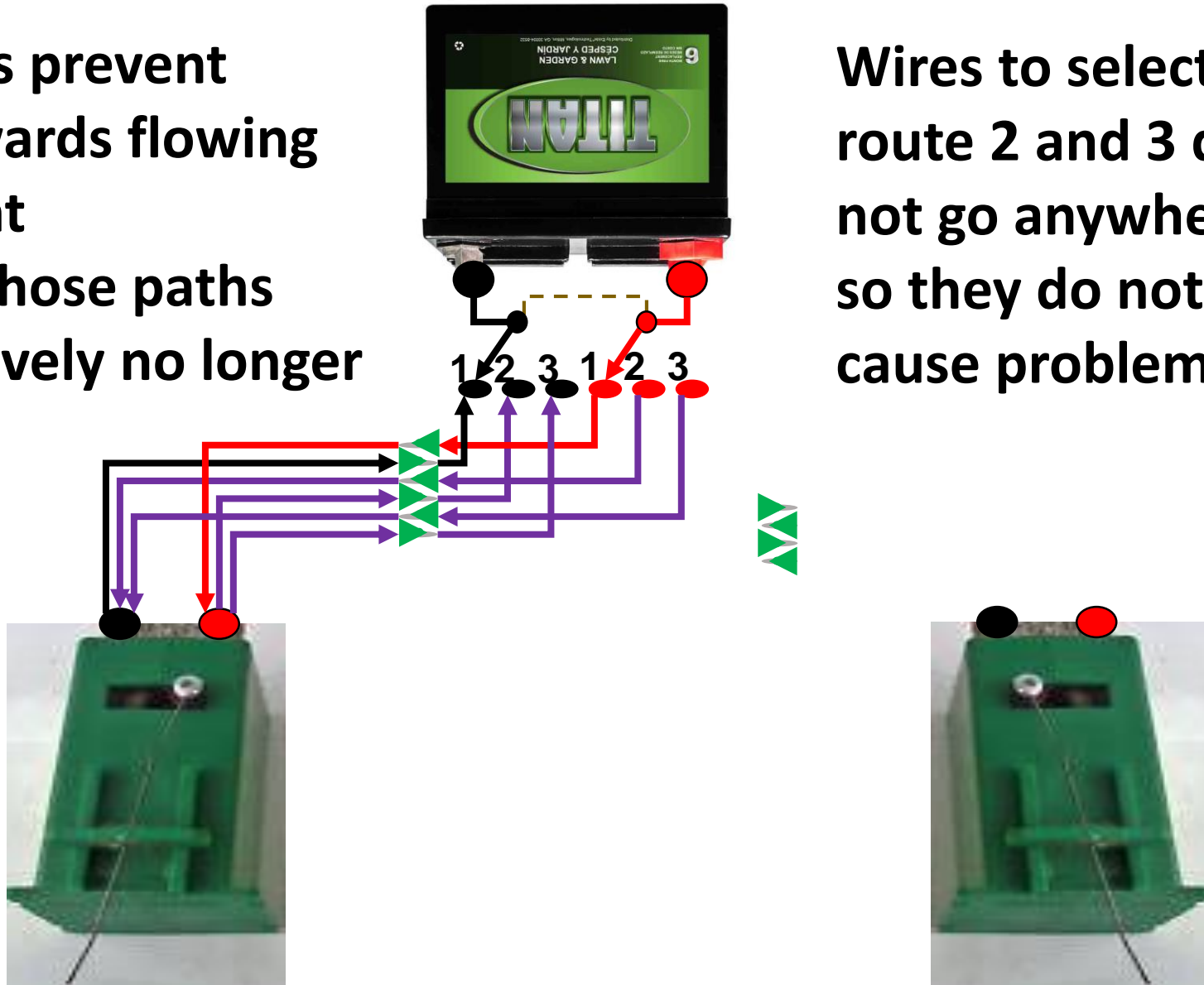Wires to selector route 2 and 3 do not go anywhere so they do not cause problems



I won't bore you


**---- with the equivalent for the other
switch positions – take my word for
it, they also work**

(Thanks accepted)

**Other positions left as an exercise
for the student**

Practical Example: Schnieder 5-track Yard Throat

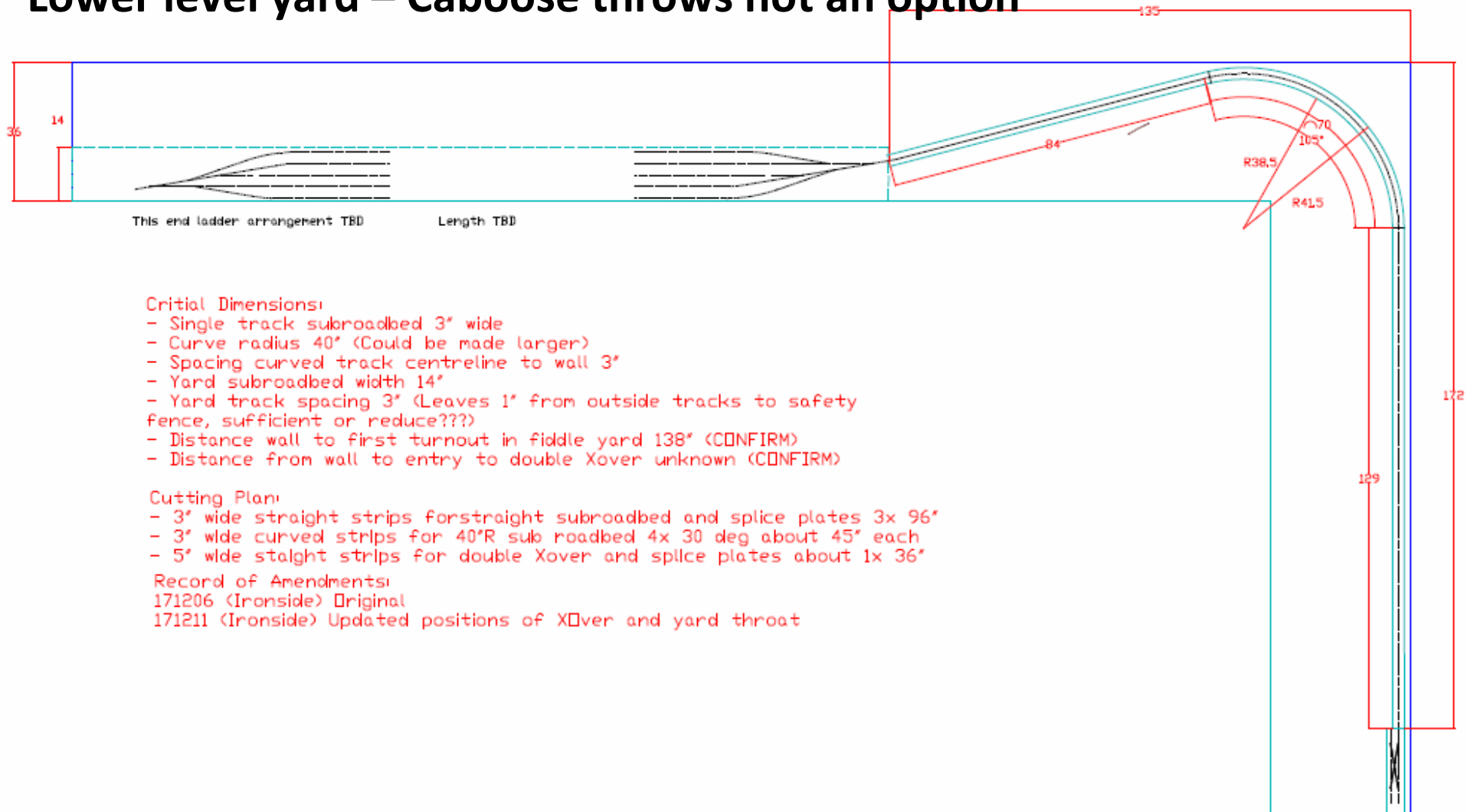
Lower level yard – Caboose throws not an option



Yard Throat



Turnout setting to track relationship

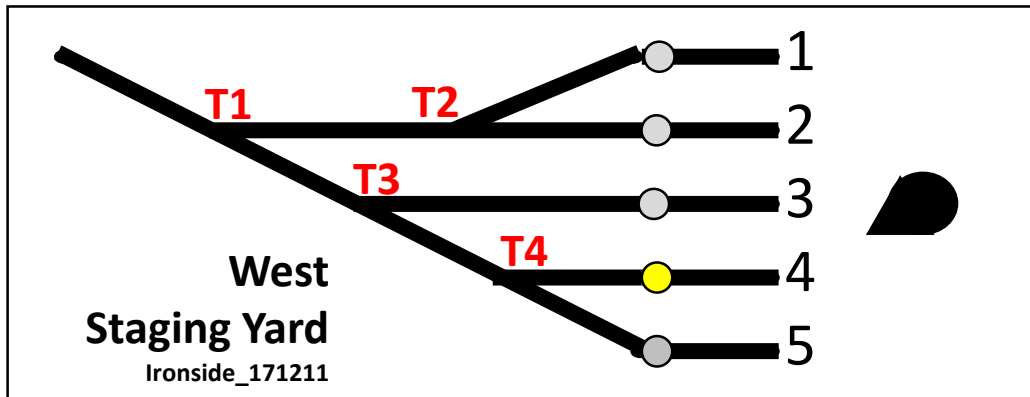

Rotary Selector set for Track 4


Route Selection

Track	T1	T2	T3	T4
1	D	D		
2	D	S		
3	S		D	
4	S		S	D
5	S		S	S

S = Straight

D = Diverging



Blanks are "Don't Care"

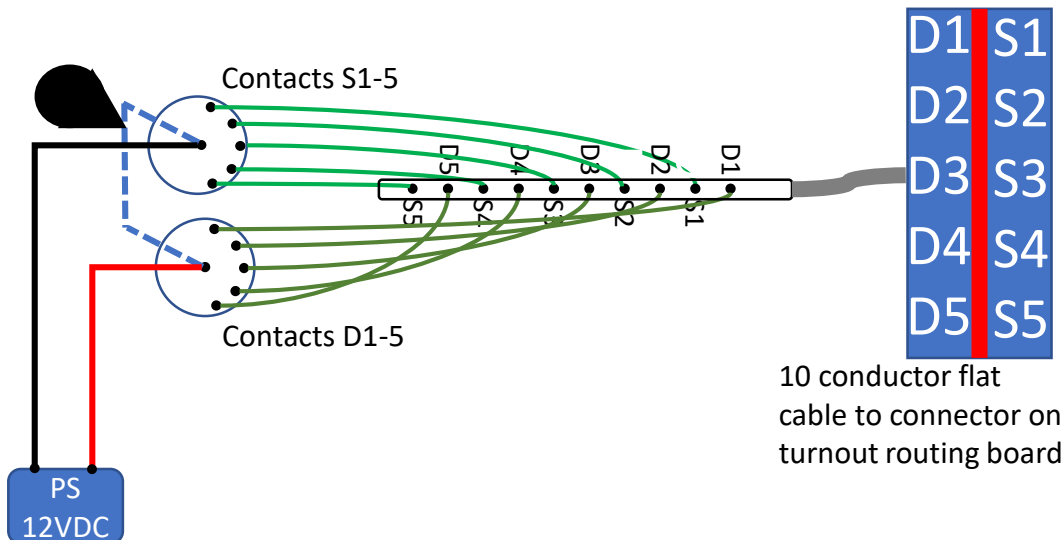

10 conductor flat cable to connector on turnout routing board


Operator Interface

Initial Design

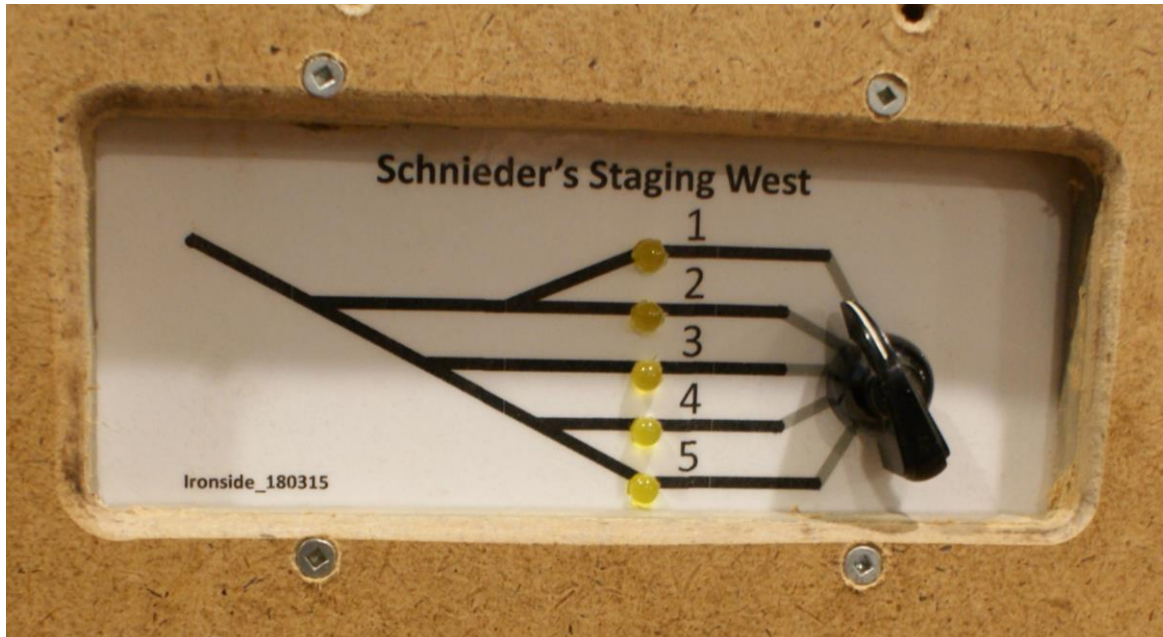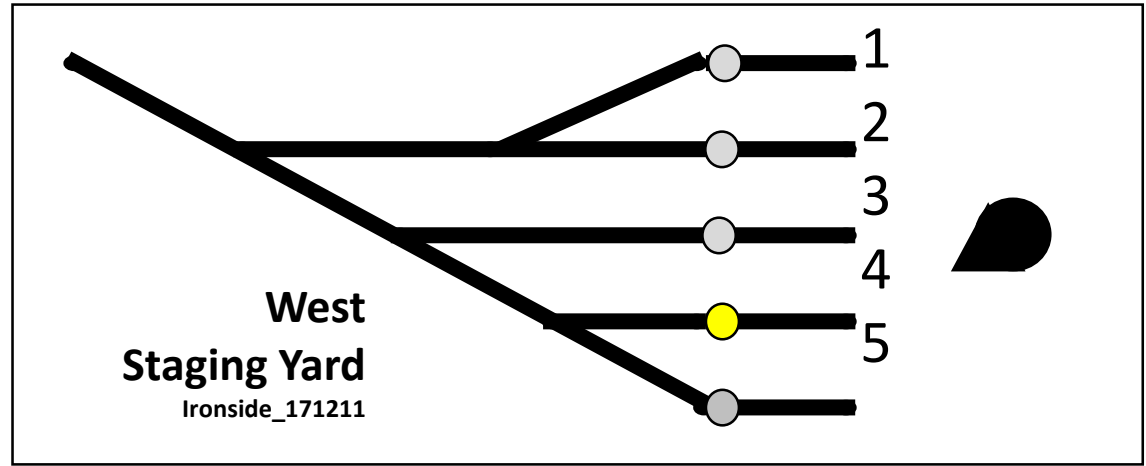

Actual

Interconnect panel – Generic design

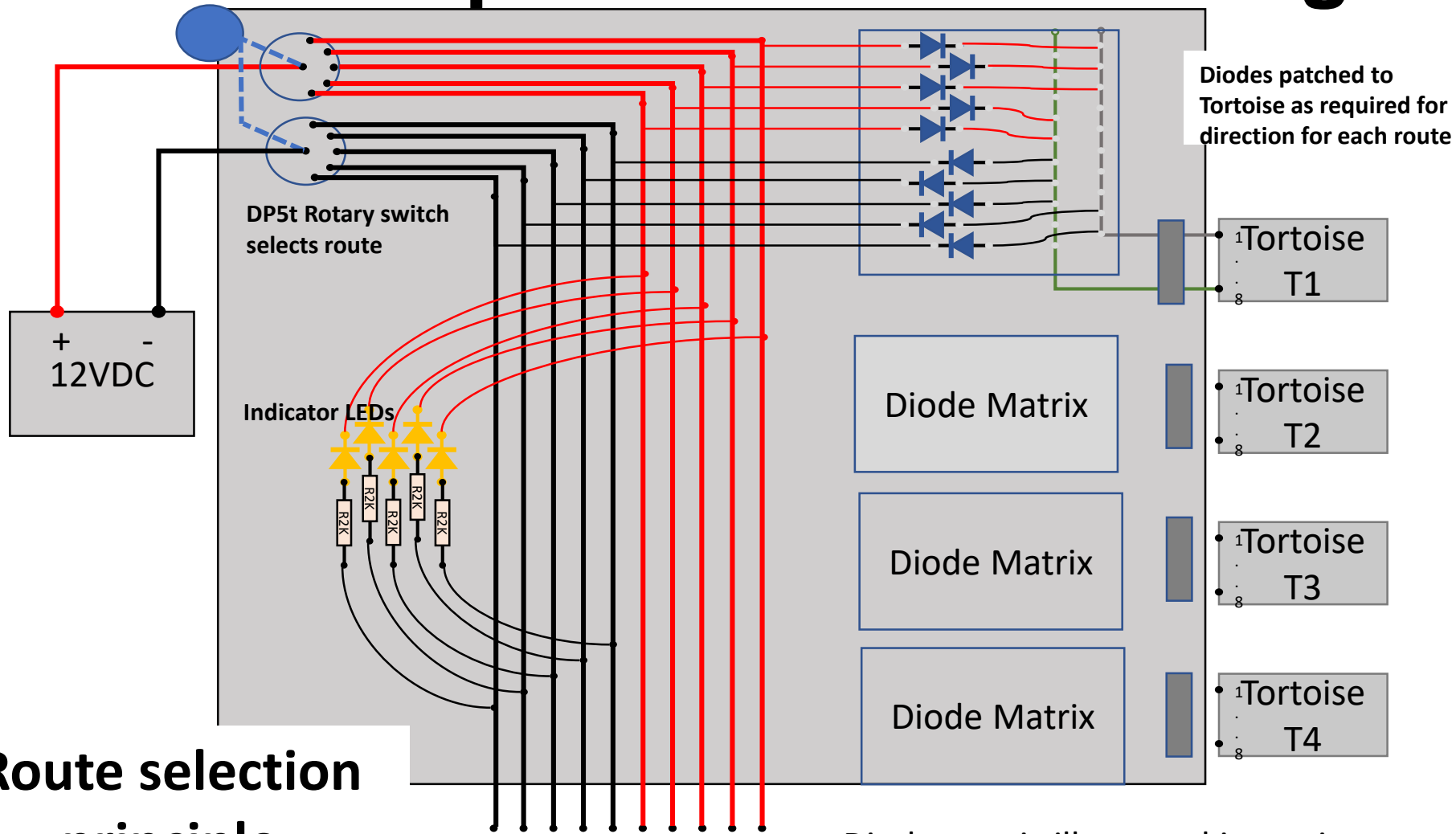

Route selection principle

Selected rotary switch wafer output contacts are connected to the power leads and others are open. Diode matrices prevent sneak paths to Tortoises


Only one +/- pair is active at a time

Diode matrix illustrated is maximum; optimization in detail design will reduce number of diodes




Interconnect - Specific design

Arrow heads indicate the banded diode lead.

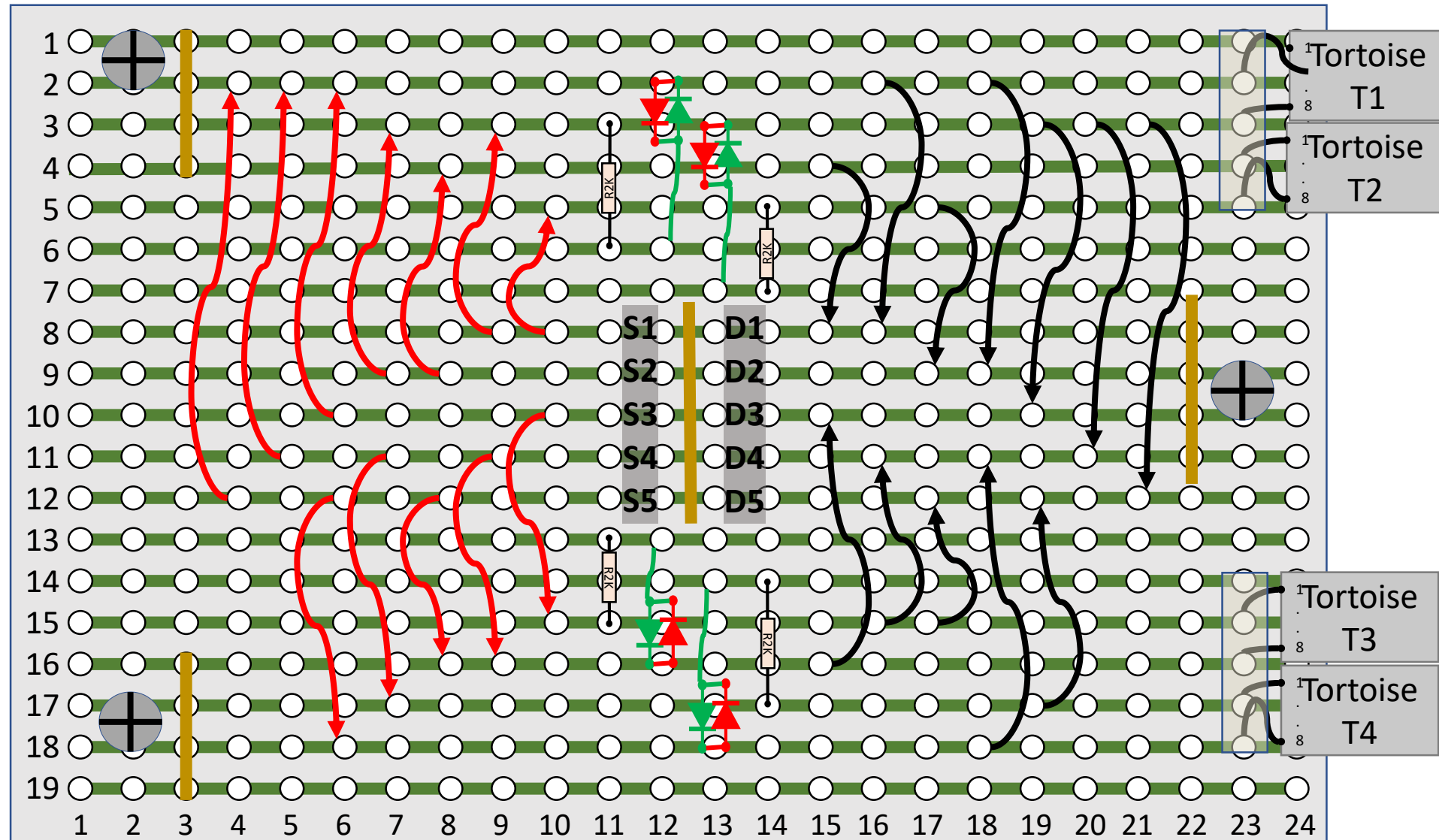
Bi-colour diodes oriented so that Red=Diverging



Interconnect panel - Actual build

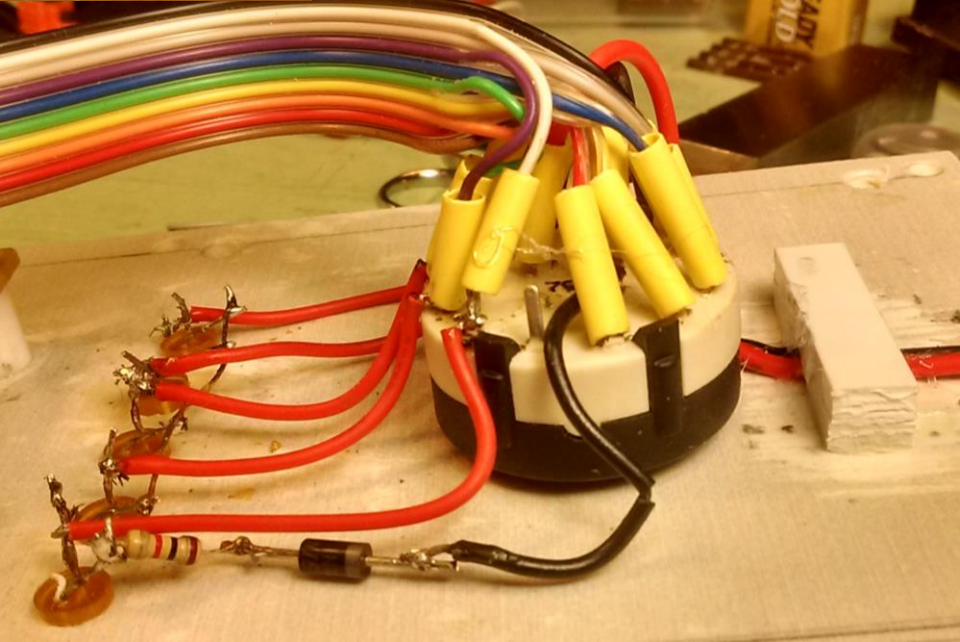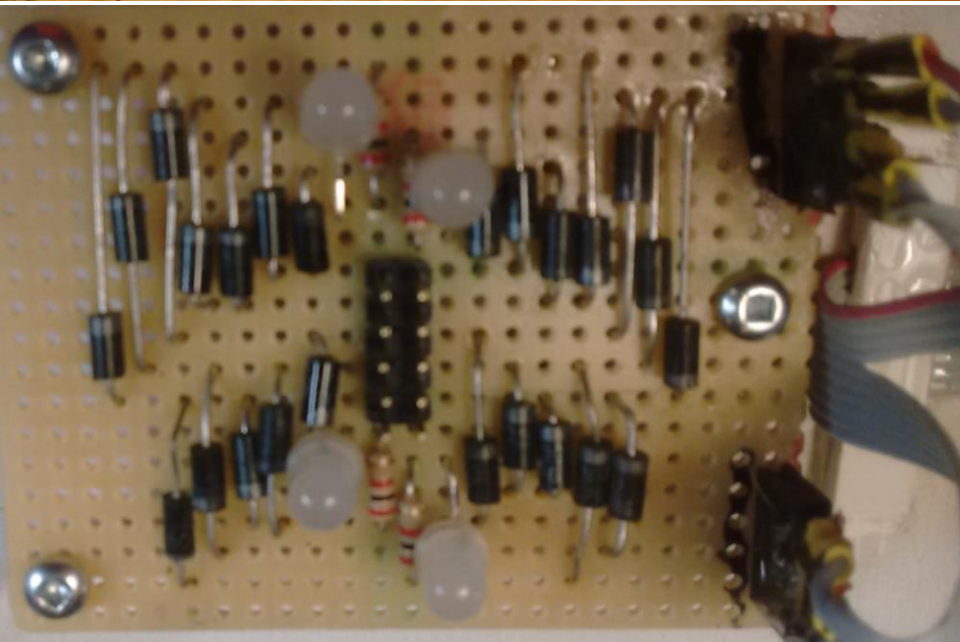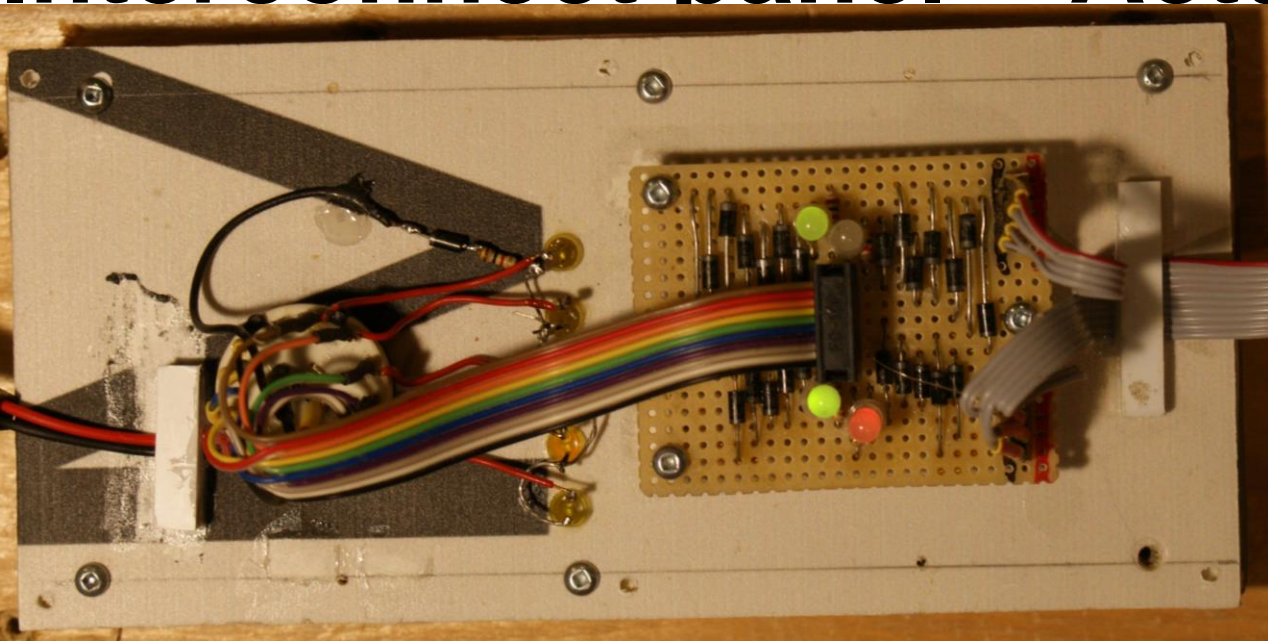

Tortoise Connection – Actual Build

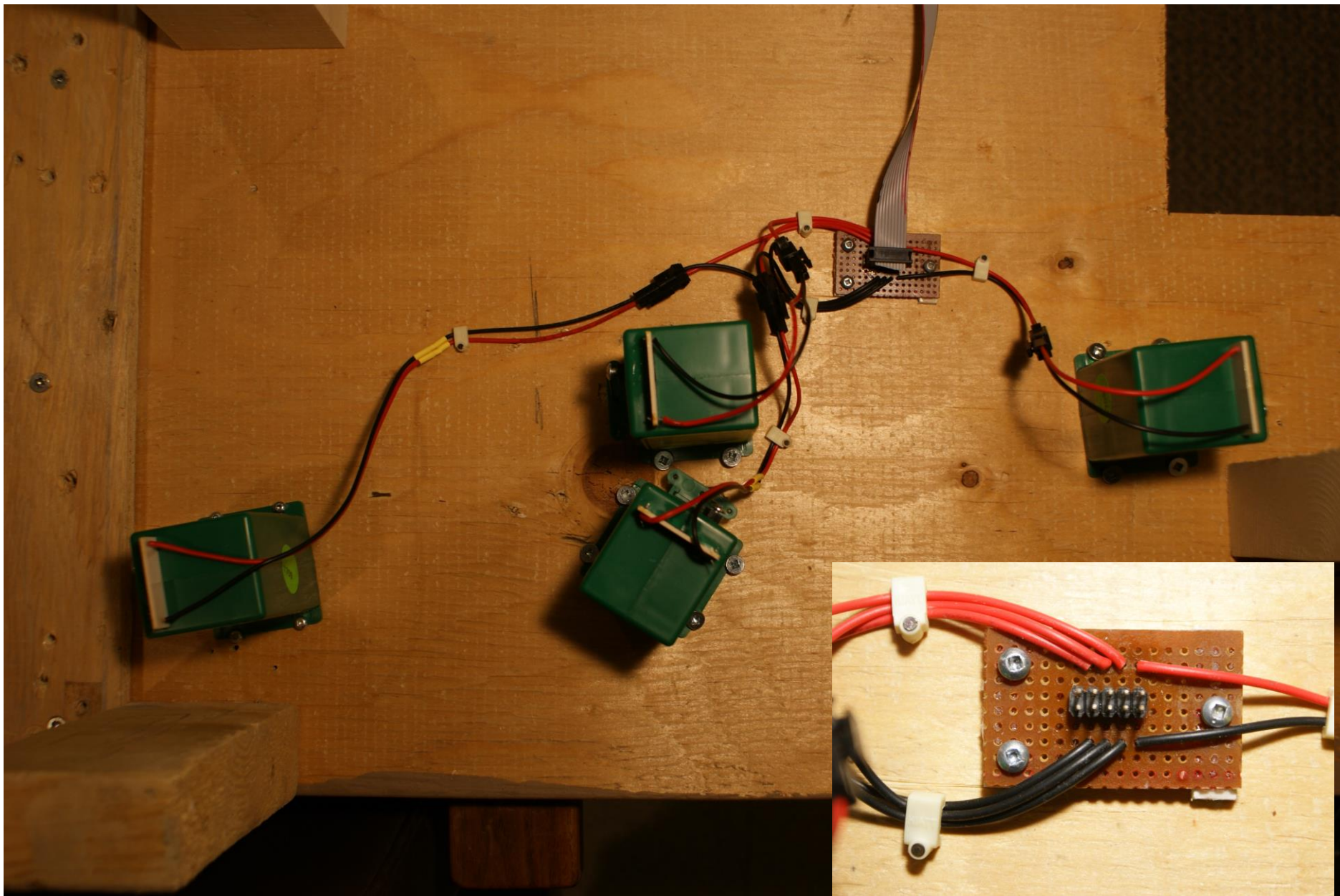

Notes on the Implementation

- **PC tracked board – ensures regular, understandable component layout**
- **Design for Maintenance – headers, flat cable, Tortoise connectors provide connections from panel to switch motors**
- **Power supply – standard wall wart or power block**
- **Bi-colour LEDs – not necessary, but useful test/diagnostic assist**
- **Tortoise wiring – done with confirmation testing that turnouts switch correct direction**

Staging Yard Throat Panel Materials

- 1/8" Plastic substrate
- Printed panel (bond to substrate)
- 1x rotary switch
- 5x LED Ye Staging
- 4x LED Bicolour Rd/Gr
- 5x Resistors
- 25x Diodes
- 1x PC Strip board Matrix
- 1x PC Strip board Tortoise connect
- 1x Header 10-way
- 1x Plug flat cable 10 way
- 5x connector pairs 2-way
- 3ft 10-way flat cable
- 6x Screw pan Robertson #4x1/2
- 4x Screw flat Robertson #6x1/2
- Wood frame

**Total cost (electronic parts from China)
about \$6**

Summary

- **Operations made simpler by making design just a bit more complicated**
- **Particularly suited for simple yard throats/ ladders**
- **Multi-turnout routing does not require complex, expensive, programmable electronics**

Contact: Jim Ironside at IronsideJim@gmail.com